APPLICATION NOTE

MIPS R4000 Slew Rate Control Logic for Output Buffers

Shabbir Latif
MIPS Technologies, Inc.
2011 N. Shoreline Blvd.
P. O. Box 7311
Mt. View, CA 94039-7311

Publication No.: AP001
Publication Date: July, 1992

MIPS Technologies, Inc. reserves the right to make changes to any products herein at any time without notice in order to improve function or design. MIPS does not assume any liability arising out of the application or use of any product or circuit described herein; neither does it convey any license under patent rights nor imply the rights of others.

Copyright 1992 by MIPS Technologies, Inc. No part of this document may be reproduced in any form or by any means without the prior written consent of MIPS Technologies, Inc.

R4000 and R4400 are registered trademarks of MIPS Technologies, Inc.

The R4000 /R4400 is available from the following manufacturers:

Integrated Device Technology, Inc. (Attention - RISC Microprocessor Marketing)
2975 Stender Way
Santa Clara, CA 95052-8015
Tel: (408) 727 6116

LSI Logic Corporation (Attention - MIPS Division)
1551 McCarthy Blvd.
Milpitas, CA 95035
Tel: (408) 433 8000

NEC Corporation (Attention - Microcomputer Division)
401 Ellis St.
Mountain View, CA 94039
Tel: (415) 960-6000

Performance Semiconductor Corporation (Attention - Microprocessor Marketing)
610 E. Weddell Drive
Sunnyvale, CA 94089
Tel: (408) 734 9000

Siemens Components Inc. (Attention - Integrated Circuit Division)
10950 Tantau Ave.
Cupertino, CA 95014
Tel: (408) 777-4500

Toshiba Corporation
9740 Irvine Blvd.
Irvine, CA 92713
(714) 583-3000

Table of Contents

1. Overview 5
2. Slew Rate Control for the Output Buffers in R4000 6
3. How to Set the “Drive off Delay” 9
4. Examples.....13
    - Example 1 13
    - Example 2 13
    - Example 3 14
    - Example 4 14
5. Summary 15
6. References.....16
7. Reader’s Comments 17

Overview

1

One of the largest causes of variation in voltage or noise on the GND and VCC supplies is the switching of the Output Buffers. This variation in supply voltages has two causes:

- the large number of buffers that can switch at the same time
- each buffer driving a large external load

Noise can be calculated using the formula

$$V = L(\Delta i/\Delta t)$$

where **V** is the noise on the supplies, **L** is the inductance of the supply pin, bonding wire, etc., and $\Delta i/\Delta t$ is the rate at which the current changes; this term is directly related to how fast the load capacitor is charged or discharged by the output drivers of the microprocessor.

The above variation or noise on the GND and VCC supplies can be reduced by increasing the rise and fall times of the output drive. Although this reduces the $\Delta i/\Delta t$ term, it also increases the propagation delay time of the output signal to its destination and care must be taken to ensure the resulting delay meets system design requirements.

Slew Rate Control for the Output Buffers in R4000

2

The R4000 has Slew Rate Control Logic with a negative feedback loop that adjusts the output buffer drive (or slew rate) so that the output buffer is fast enough to meet the system's speed requirement, and no more, in order to minimize the noise for that particular system. As shown in Figure 1, the feedback loop includes path (A) from pins **IO_Out** to **IO_In**. This path represents the signal path with the longest delay from the R4000 to any other external register which matches the load and the transmission line effect on the PCB (see Reference 1). The Slew Rate Control Logic drives a signal through the **IO_Out** output buffer and, using a selectable clock, samples the return signal on the **IO_In** pin. If the signal arrives earlier than the maximum acceptable delay, which is selected by the designer, the Slew Rate Control Logic slows the speed of the **IO_Out** output buffer; if the signal arrives later, it speeds up the **IO_Out** output buffer.

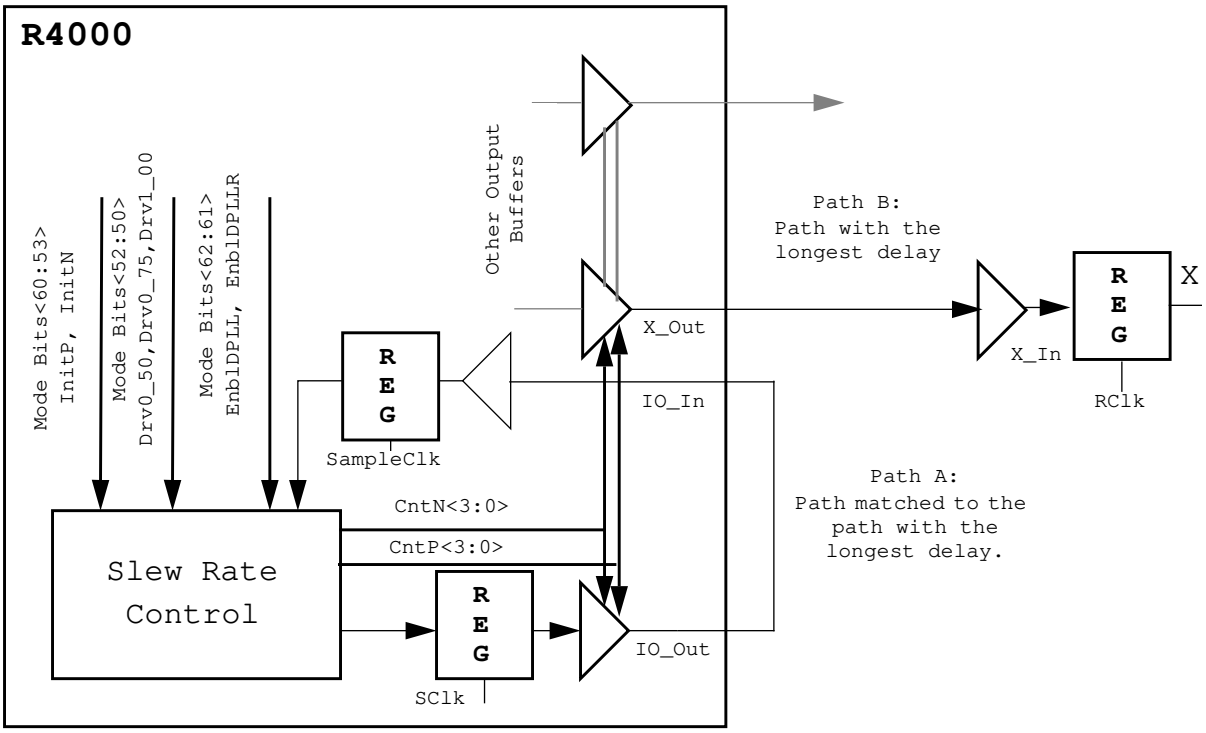

Figure 1: Overview of the Slew Rate Control Mechanism in R4000

The Slew Rate Control Logic uses the signals **CntN<3:0>** and **CntP<3:0>** to control the N-channel and the P-channel devices, respectively, of the predrivers to the final stage of the output buffers. This allows **CntN<3:0>** signals to adjust the rising edge of the outputs and **CntP<3:0>** to adjust the falling edge, giving 16 independent states of control in each direction. All ones on **CntN<3:0>** provides the fastest pullup rate and all zeros on **CntP<3:0>** provides the fastest pulldown rate. The variation in the least significant bit (LSB), **CntN<0>** or **CntP<0>**, provides the smallest resolution. Note that there is always some jitter at the output due to the fact that the control mechanism is continuously trying to converge to the programmed maximum adjustable delay value by switching the state of the LSBs **CntN<0>** and **CntP<0>**. The signals, **CntN<3:0>** and **CntP<3:0>**, that control the output buffer for **IO_Out** pin also control the output buffers for the rest of the pins of the R4000. Thus, the slew rate of the rest of the output buffers will vary in the same manner as the variation of the **IO_OUT** buffer; however, the amount of variation will depend on the external loading on each pin.

The R4000 has three modes for controlling the slew rates of the output buffers and in turn minimizing the noise caused by $\Delta i/\Delta t$. As shown in Table 1, these three modes are selected by Mode Bits<62:61>, **EnblDPLL** and **EnblDPLLR**, respectively.

Table 1: Modes of Operation for Controlling the Slew Rate

EnblDPLL	EnblDPLLR	Modes of Operation
0	*0*	*Keep the slew rate of the output drivers **fixed** as set by the Mode Bits<60:57> and <56:53>, **programmed during boot time**.*
0	*1*	*Enable the mechanism to **dynamically control** the slew rate **only during ColdReset** and thereafter retain the slew rate of the output drivers.*
1	*X (don't care)*	*Enable the mechanism to **dynamically control** the slew rate **during ColdReset and Normal Operation**.*

The first mode in Table 1, which keeps the slew rate of the output buffer fixed, is useful for the situation in which any jitter associated with the operation of the slew rate control mechanism cannot be tolerated, and the variation in temperature and supply voltage after ColdReset is expected to be small.

To dynamically control the slew rate, either during the ColdReset operation or during both ColdReset and Normal operations, the R4000 does the following.

1. It uses Mode Bits<60:57> and <56:53> (also referred as **InitP** and **InitN**, respectively), programmed during the boot time, to set the initial values of **CntN<3:0>** and **CntP<3:0>**, which in turn sets the initial slew rate of the output buffers.
2. It uses the "drive-off" delay, programmed at boot time through Mode Bits <52:50> (**Drv1_00**, **Drv0_75** or **Drv0_50**), as the maximum acceptable delay of the data and, accordingly, selects the SampleClk to sample the **IO_In** as shown in Figure 1. Table 2 shows the truth table for Mode Bits<52:50>; the remaining combinations are reserved
3. It uses the path between **IO_Out** pin and **IO_In** pin, as described earlier.

Table 2: The Truth Table for Mode Bits <52:50> , Setting Drive-off Delays

Mode	Drv1_00	Drv0_75	Drv_5	Drive-off time
Dynamic	*0*	*0*	*1*	*$0.50*T^{(2)}$*
Dynamic	*0*	*1*	*0*	*$0.75*T^{(2)}$*
Dynamic	*1*	*0*	*0*	*$1.00*T^{(2)}$*
Fixed	*X*	*X*	*X*	*Note 1*

Notes: 1) The Fixed "Drive-off" Time Is Selected By Initn and Initp (Mode Bits<60:53>).
2) 'T' is the period of the Master clock (MasterClk).

To make the programmed delay value independent of system clock frequency (**MasterClk**), the delay value is specified in terms of a percentage of one cycle time instead of a constant. Also, note that this mechanism is not affected by the interface clocks divisor (Mode Bits<49:47>), it is always a fraction of one (**MasterClk**) cycle.

How to Set the “Drive off Delay”

3

As mentioned in the previous section, for the dynamic control of the output buffer slew rate, R4000 uses the “drive off delay” programmed by Mode Bits<52:50> during boot time . This section explains how to determine the setting of these mode bits. In general, a path is selected (Path B in Figure 1) with the longest delay from the output pin to the output of the receiving data register (node X in Figure 1). Then, the transmission line effect and the capacitive loading of the **IO_Out** is matched with the transmission line effect and the capacitive loading of Path B (see Reference 1 for detail). Finally, after calculating at what time the **SampleClk** in the Path A should be, the appropriate Mode Bits<52:50> (**Drv1_00**, **Drv0_75** or **Drv0_50**) are selected.

Figure 2 shows the Path A again and the corresponding timing diagram with all the delay components labelled. The equation of the delay T_{SS} plus the clock jitter T_{SSj} in terms of the output buffer delay (t_{DO}) is also shown (Equation 1). T_{SS} is the time from the rising edge of the **SClk**, which triggers the **IO_Out,** to the **SampleClk** edge which latches the **IO_In** at a selected time. T_{SSj} is the jitter of the **SampleClk** with reference to the **SClk.** The T_{SSj} could be both positive or negative; however, a positive number is chosen because, in this case its affect is worse than the affect of a negative number. t_{DOj} is the jitter on the output caused by the slew rate control logic which is continuously trying to converge to the programmed “drive off” delay value by switching the state of the LSBs, **CntN<0>** and **CntP<0>**.

Figure 3 shows Path B again and corresponding timing diagram with all the delay components labelled. This path is an example of a signal path from the R4000 to a receive-data register. This register could be part of external agent chip or an individual component on the PCB. The rising edge of **SClk** drives the data, and the rising edge of the **RClkD** latches the data into the register. T_{SR} is the delay between the **RClk** and the **SClk**, T_{SRD} is delay between the **RClkD** and the **SClk** and T_{SRj} is the jitter on **RClk** or **RClkD** with respect to **SClk**. The T_{SRDj} could be a positive or a negative number; however, a negative number chosen because , in this case, its affect is worse than the affect of a positive number. The equation of the delay time T_{SRD} is shown in Equation 2 in Figure 3.

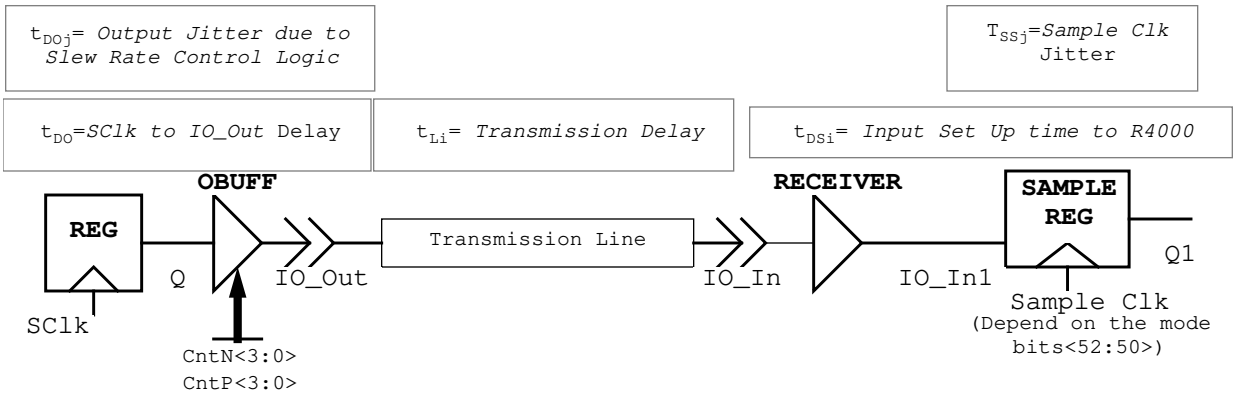

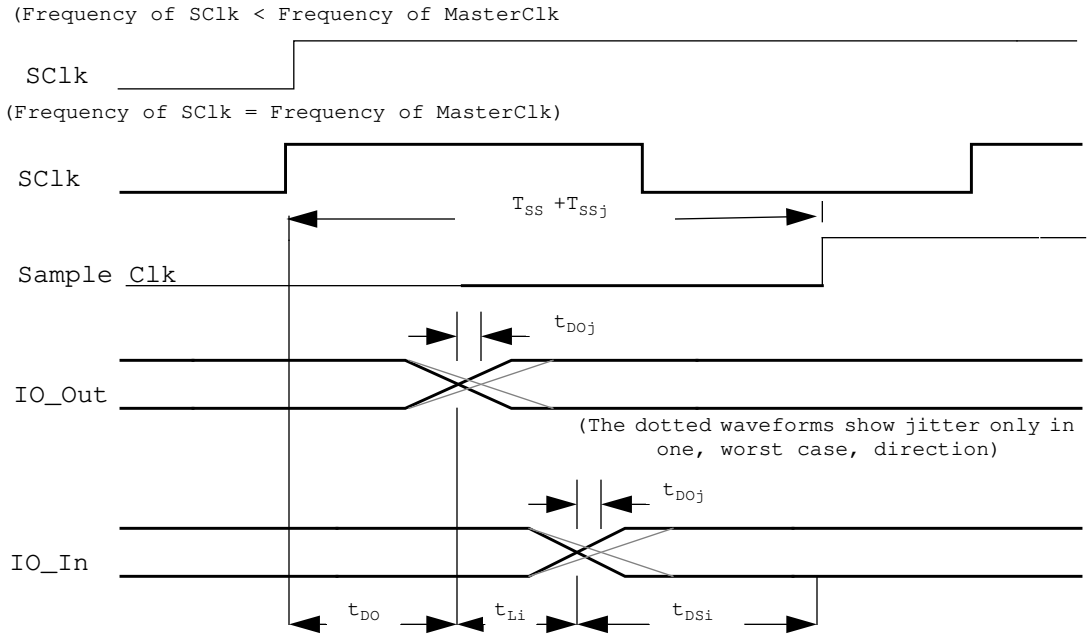

$$Eq\ 1:\ T_{SS} + T_{SSj} = t_{DO} + t_{Li} + t_{DSi}$$

Figure 2: Path from pins IO_Out to IO_In.

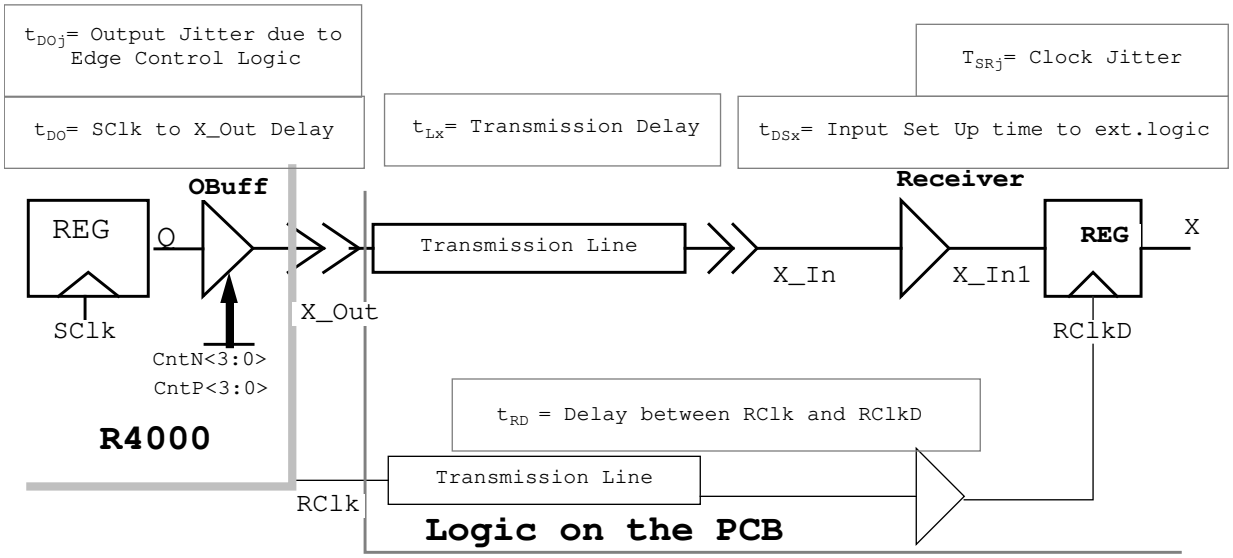

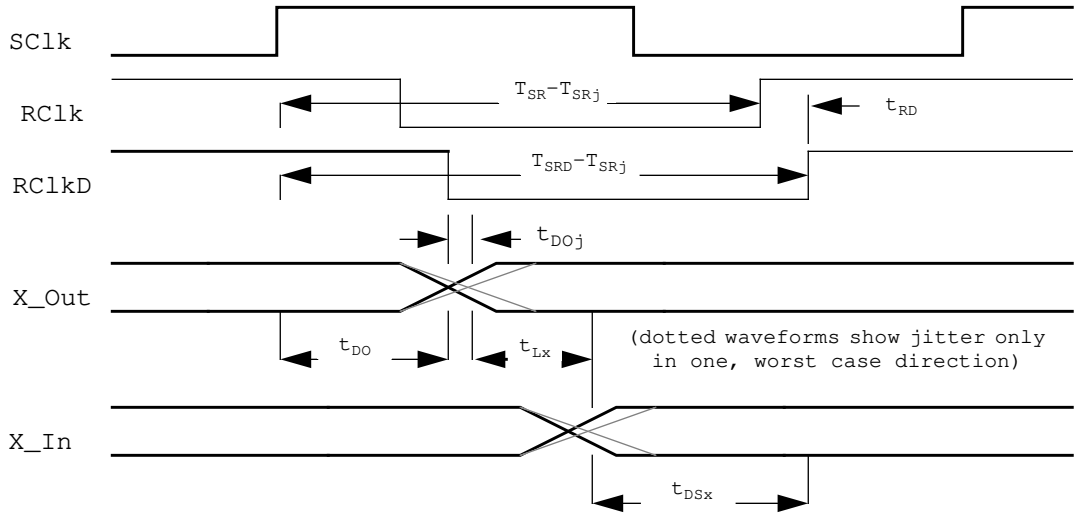

$$Eq\ 2:\ T_{SRD}-T_{SRj} = t_{DO} + t_{DOj} + t_{Lx} + t_{DSx}$$

Figure 3: Representative Worst Case Path from R4000 to External Component

If the capacitive load and the transmission line between the pins **IO_Out** and **IO_In** are matched with the loading and the transmission line between **X_Out** and **X_In**, then the output buffer delay, t_{DO}, is equal in both the paths, and $t_{Li} = t_{Lx}$. Thus, deriving t_{DO} from the Equation 2 and substituting into the equation Equation 1, T_{SS} can be derived to decide which of the Mode Bits **Drv1_00**, **Drv0_75**, or **Drv0_50** needs to be selected.

Eq 3: DrvX_XX $< T_{SS} = T_{SRD} - T_{SRj} - t_{SSj} + t_{DSi} - t_{DSx} - t_{DOj}$

Examples

4

The following examples show how to set Mode Bits <52:50>.

Example 1

In a system with **SysCkRatio** (Mode bits<17:15>) set to 0 (Ref: 1) , the frequency of **RClk** is equal to the frequency of **MasterClk**. If the delay, equal to the delay between **RClk** and **RClkD**, is added between **SyncIn** pin and **SyncOut** pin, the **RClkD** is locked to the **MasterClk**. But since **RClkD** leads **SCLk** and **MasterClk** by 0.25*T; this means, T_{SRD} is (0.75*T).

The R4000 AC specification (Ref.1) shows clock jitter = 0.5 ns, data set up time = 5.0 ns, and t_{DOj} = 1 ns. Assuming t_{DSX} = 7 ns, Equation 3 can be rewritten as:

$$Eq\ 4:\ T_{SS} = (0.75*T) - 0.5ns - 0.5ns + 5\ ns - 7ns - 1ns = 0.75*T - 4ns$$

Thus, for a 50 MHz system, T_{SS} would be 11 ns; so Drv0_50 would be set to 1.

Example 2

In a system with **SysCkRatio** (Mode bits<17:15>) set to 0, the frequency of the **RClk** is equal to the frequency of **MasterClk**. If the **Sync_In** pin is shorted to the **SyncOut** pin, the **RClk** is locked to the **MasterClk**. Since **RClk** leads **SClk** and **MasterClk** by 0.25*T; this means, T_{SRD} is equal to (0.75*T + t_{RD}), where t_{RD} is the delay between **RClk** and **RClkD**. Thus, Equation 4, from Example 1, can be rewritten as,

$$T_{SS} = (0.75*T + t_{RD}) - 4ns$$

If t_{RD} > 4ns then T_{SRD} could be > (0.75*T+4ns), making T_{SS} > 0.75*T; in which case **Drv0_75** is set to 1.

Example 3

In a system with **SysCkRatio** set to 1, the frequency of **RClk** is two-thirds the frequency of **MasterClk**, so T_{SRD} is equal to (1.0*T) given in Example 1, and T_{SRD} is greater than (1.0*T) given in Example 2.

Thus, in the first example **Drv0_75** is set to 1, and in the second example **Drv1_00** is set to 1.

Example 4

Similarly, in the system with the **SysCkRatio** set to 2, the frequency of **RClk** is half the frequency of **MasterClk**; so **Drv1_00** is set to 1 in Examples 1 and 2.

Summary

5

The R4000 has Slew Rate Control Logic with negative feedback loop that adjusts the output buffer drive so that the output buffer is only fast enough to meet the system's speed requirement, and no more, in order to minimize the noise for that particular system. The maximum acceptable delay is programmed at the boot time using the "drive-off" Mode Bits<52:50> (**Drv1_00**, **Drv0_75** or **Drv0_50**). It also provides the flexibility to select whether to enable the control only during the ColdReset time, or during the ColdReset time and the Normal operation, or to select a fixed slew rate as programmed by the Mode Bits<60:53> (**InitP** and **InitN**). Some examples were shown in this document on how to select the "drive-off" delay mode bits.

References

Reference 1: MIPS R4000 Processor Interface Specification
Reference 2: MIPS R4000 Microprocessor User's Manual

Reader's Comments

Please FAX your comments about this document to:

Anjaneya Thakar
Fax: (415) 390-6170
Address: 2011 N. Shoreline Blvd., P.O. Box 7311, Moutain View, CA 94039-7311

Areas of Improvement:

Errors:

Reader Information:

Name:
Company:
Address:
Phone:
FAX:

Thank you for your feedback.